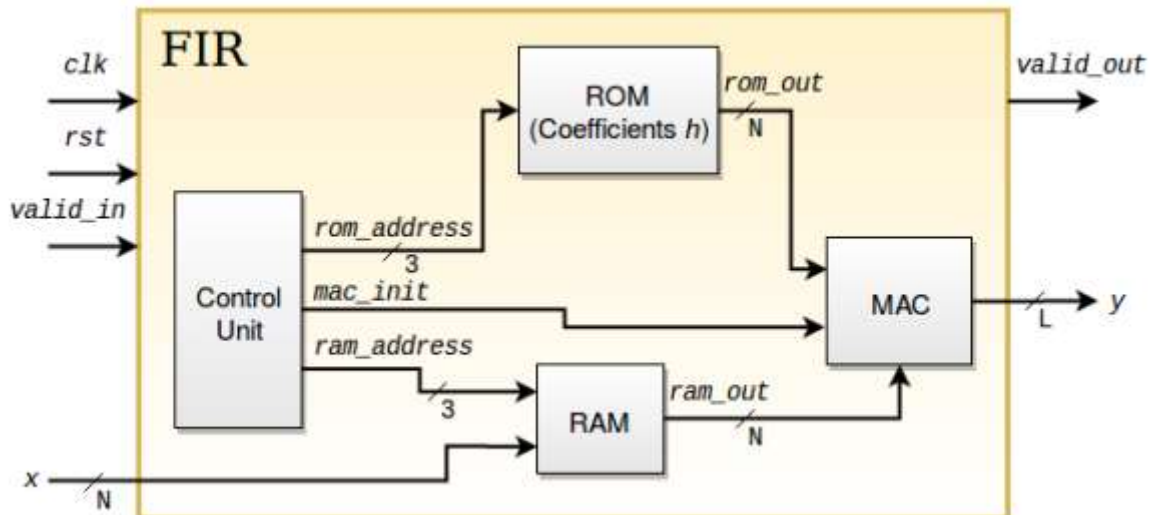


## FIR Φίλτρο

Για την περιγραφή του φίλτρου βασιστήκαμε στο παρακάτω σχήμα:



Προκειμένου να περιγράψουμε το παραπάνω κύκλωμα με Structural αρχιτεκτονική, δημιουργήσαμε τις εξής οντότητες:

- **D Flip-Flop** (καθυστέρησης 1 κύκλου)

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity d1 is
    Port(
        Clk, reset, D: in std_logic;
        Q: out std_logic
    );
end d1;

architecture Behavioral of d1 is
    signal rst: std_logic;
begin
    process(Clk, reset)
    begin
        if reset='1' then rst <= '1';
        elsif (Clk'event and Clk='1') then
            if rst='1' then Q <= '0'; rst <= '0';
            else Q <= D;
            end if;
        end if;
    end process;
end Behavioral;
```

## 4η εργαστηριακή άσκηση

- Control Unit - Μονάδα Ελέγχου

```
library ieee;
use ieee.std_logic_1164.all;
use ieee.std_logic_unsigned.all;

entity control_unit is
    port (
        clk : in std_logic;
        reset : in std_logic;
        valid_in: in std_logic;
        mac_init : out std_logic;
        we, en: out std_logic;
        rom_address : out std_logic_vector(2 downto 0);
        ram_address : out std_logic_vector(2 downto 0)
    );
end entity control_unit;

architecture control_unit_arch of control_unit is
    signal counter : std_logic_vector(2 downto 0):="000"; -- Counter for ROM and RAM
begin
    process (clk, reset)
    begin
        if reset = '1' then
            counter <= "000"; -- Reset counter
        elsif rising_edge(clk) then
            if counter="000" then
                if valid_in='1' then
                    mac_init <= '1'; -- Initialize mac unit
                    we <= '1'; en <= '1'; -- Write x to RAM[0]
                    rom_address <= std_logic_vector(counter);
                    ram_address <= std_logic_vector(counter);
                    counter <= counter + 1;
                else
                    we <= '0'; en <= '0'; -- Input is invalid, disable access to RAM
                    mac_init <= '1';
                end if;
            else
                we <= '0'; en <= '1'; -- Read RAM[1-7]
                mac_init <= '0';
                rom_address <= std_logic_vector(counter);
                ram_address <= std_logic_vector(counter);
                counter <= counter + 1;
            end if;
        end if;
    end process;
end architecture control_unit_arch;
```

## 4η εργαστηριακή άσκηση

- Μνήμη ROM

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use ieee.std_logic_unsigned.all;

entity mlab_rom is
    generic (
        coeff_width : integer :=8      --- width of coefficients (bits)
    );
    Port ( clk : in  STD_LOGIC;
          en : in  STD_LOGIC;          --- operation enable
          addr : in  STD_LOGIC_VECTOR (2 downto 0);      -- memory address
          rom_out : out STD_LOGIC_VECTOR (coeff_width-1 downto 0)); -- output data
end mlab_rom;

architecture Behavioral of mlab_rom is

    type rom_type is array (7 downto 0) of std_logic_vector (coeff_width-1 downto 0);
    signal rom : rom_type:= ("00001000", "00000111", "00000110", "00000101",
                             "00000100", "00000011", "00000010", "00000001");
    -- initialization of rom with user data

    signal rdata : std_logic_vector(coeff_width-1 downto 0) := (others => '0');
begin

    rdata <= rom(conv_integer(addr));

    process (clk)
    begin
        if (clk'event and clk = '1') then
            if (en = '1') then
                rom_out <= rdata;
            end if;
        end if;
    end process;

end Behavioral;
```

## 4η εργαστηριακή άσκηση

- Μνήμη RAM

```
library ieee;
use ieee.std_logic_1164.all;
use ieee.std_logic_unsigned.all;

entity mlab_ram is
    generic (
        data_width : integer := 8          --- width of data (bits)
    );
    port (clk : in std_logic;
          reset: in std_logic;
          we   : in std_logic;             --- memory write enable
          en   : in std_logic;             --- operation enable
          addr : in std_logic_vector(2 downto 0);    -- memory address
          di   : in std_logic_vector(data_width-1 downto 0);    -- input data
          do   : out std_logic_vector(data_width-1 downto 0));    -- output data
end mlab_ram;

architecture Behavioral of mlab_ram is

    type ram_type is array (7 downto 0) of std_logic_vector (data_width-1 downto 0);
    signal RAM : ram_type := (others => (others => '0'));

begin

    process (clk, reset)
    begin
        if reset='1' then -- Initialize RAM with all zeroes
            for i in 7 downto 0 loop
                RAM(i) <= "00000000";
            end loop;
        elsif clk'event and clk = '1' then
            if en = '1' then
                if we = '1' then -- write operation
                    for i in 6 downto 0 loop
                        RAM(i+1) <= RAM(i);    -- shift previous RAM entries
                    end loop;
                    -- Write new data to RAM at address 0
                    RAM(0) <= di;
                    do <= di;
                else -- read operation
                    do <= RAM(conv_integer(addr));
                end if;
            end if;
        end if;
    end process;

end Behavioral;
```

## 4η εργαστηριακή άσκηση

- MAC - Μονάδα Πολλαπλασιασμού με Συσσώρευση

```
library ieee;
use ieee.std_logic_1164.all;
use ieee.std_logic_unsigned.all;

entity mac_unit is
    port (
        clk : in std_logic;
        rom_out : in std_logic_vector(7 downto 0); -- Coefficients from ROM
        ram_out : in std_logic_vector(7 downto 0); -- Input data from RAM
        mac_init : in std_logic; -- Initialization signal
        valid_out: out std_logic := '0';
        y_out : inout std_logic_vector(18 downto 0) -- Output
    );
end entity mac_unit;

architecture mac_unit_arch of mac_unit is
    signal sum: std_logic_vector(18 downto 0);
begin
    process (clk)
    begin
        if rising_edge(clk) then
            if mac_init = '1' then
                sum <= "000" & rom_out*ram_out;
                y_out <= sum;
                if sum/="U" then valid_out <= '1'; end if;

            elsif mac_init = '0' then
                sum <= sum + ram_out*rom_out; -- Add to partial sum computed product
                valid_out <= '0';

            end if;
        end if;
    end process;
end mac_unit_arch;
```

## 4η εργαστηριακή άσκηση

Χρησιμοποιώντας τις παραπάνω οντότητες και προσθέτοντας τις κατάλληλες καθυστερήσεις όπου χρειαζόταν (πχ mac\_init από το Control Unit στη MAC), προκύπτει η εξής περιγραφή του FIR φίλτρου:

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity fir_filter is
  port (
    clk, reset, valid_in: in std_logic;
    x: in std_logic_vector(7 downto 0);    -- Filter input
    valid_out: out std_logic;
    y: inout std_logic_vector(18 downto 0) -- Filter output
  );
end fir_filter;

architecture fir_filter_arch of fir_filter is
  component mac_unit is
    port (
      clk : in std_logic;
      rom_out : in std_logic_vector(7 downto 0);
      ram_out : in std_logic_vector(7 downto 0);
      mac_init : in std_logic;
      valid_out: out std_logic;
      y_out : inout std_logic_vector(18 downto 0)
    );
  end component;

  component control_unit is
    port (
      clk : in std_logic;
      reset : in std_logic;
      valid_in: in std_logic;
      mac_init : out std_logic;
      we, en: out std_logic;
      rom_address : out std_logic_vector(2 downto 0);
      ram_address : out std_logic_vector(2 downto 0)
    );
  end component;

  component mlab_ram is
    generic (
      data_width : integer :=8
    );
    port (clk : in std_logic;
          reset: in std_logic;
          we : in std_logic;
          en : in std_logic;
          addr : in std_logic_vector(2 downto 0);
          di : in std_logic_vector(data_width-1 downto 0);
```

## 4η εργαστηριακή άσκηση

```
        do : out std_logic_vector(data_width-1 downto 0));
end component;

component mlab_rom is
generic (
    coeff_width : integer :=8
);
port ( clk : in  STD_LOGIC;
      en : in  STD_LOGIC;
      addr : in  STD_LOGIC_VECTOR (2 downto 0);
      rom_out : out  STD_LOGIC_VECTOR (coeff_width-1 downto 0));
end component;

component D1 is
port (
    reset, Clk, D: in std_logic;
    Q: out std_logic
);
end component;

signal rom_out, ram_out: std_logic_vector(7 downto 0);
signal rom_ad, ram_ad: std_logic_vector(2 downto 0);
signal mac_i, mac_ii, we, en: std_logic;
begin
    control: control_unit port map(clk => clk, reset => reset, valid_in => valid_in,
                                   mac_init => mac_i, rom_address => rom_ad,
                                   ram_address => ram_ad, we => we, en => en);
    mac_in_delay: D1 port map (clk => clk, D => mac_i, Q => mac_ii, reset => '0');
    -- Delay mac_init signal one cycle to synchronize operations
    ram: mlab_ram generic map(data_width => 8)
        port map(clk => clk, reset => reset,
                 we => we, en => en, addr => ram_ad, di => x, do => ram_out);
    rom: mlab_rom generic map(coeff_width => 8)
        port map(clk => clk, en => en, addr => rom_ad, rom_out => rom_out);
    mac: mac_unit port map (clk => clk, rom_out => rom_out, ram_out => ram_out,
                           valid_out => valid_out, mac_init => mac_ii, y_out => y);
end fir_filter_arch;
```

## 4η εργαστηριακή άσκηση

Προκειμένου να ελέγξουμε την σωστή λειτουργία του κυκλώματος, γράφουμε το εξής testbench:

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.NUMERIC_STD.ALL;

entity fir_filter_tb is
end fir_filter_tb;

architecture tb_arch of fir_filter_tb is
    signal clk, reset, valid_in : std_logic;
    signal x : std_logic_vector(7 downto 0);
    signal valid_out : std_logic;
    signal y : std_logic_vector(18 downto 0);

    -- Component declaration for the DUT
    component fir_filter is
        port (
            clk, reset, valid_in: in std_logic;
            x: in std_logic_vector(7 downto 0);
            valid_out: out std_logic;
            y: inout std_logic_vector(18 downto 0)
        );
    end component;

    type input_array is array (0 to 19) of integer range 0 to 255;
    constant input_data : input_array := (208, 231, 32, 233, 161, 24, 71, 140, 245,
                                            247, 40, 248, 245, 124, 204, 36, 107, 234,
                                            202, 245);

begin
    -- DUT instantiation
    DUT: fir_filter port map (
        clk => clk,
        reset => reset,
        valid_in => valid_in,
        x => x,
        valid_out => valid_out,
        y => y
    );
    check: process
    begin

        for i in 0 to 8 loop
            x <= std_logic_vector(to_unsigned(input_data(i), x'length));
            valid_in <= '1';
            clk <= '0'; wait for 5 ns; clk <= '1'; wait for 5 ns;
            valid_in <= '0';
            for i in 6 downto 0 loop
                clk <= '0'; wait for 5 ns;
                clk <= '1'; wait for 5 ns;
            end loop;
        end loop;
    end process;
end;
```




## 4η εργαστηριακή άσκηση

```
clk <= '0'; reset <= '1'; wait for 2 ns; reset <= '0'; -- Reset filter
x <= std_logic_vector(to_unsigned(input_data(9), x'length));
valid_in <= '1';
wait for 3 ns; clk <= '1'; wait for 5 ns;
valid_in <= '0';
for i in 6 downto 0 loop
    clk <= '0'; wait for 5 ns;
    clk <= '1'; wait for 5 ns;
end loop; wait for 3 ns;

for i in 10 to 11 loop
    x <= std_logic_vector(to_unsigned(input_data(i), x'length));
    valid_in <= '1';
    clk <= '0'; wait for 5 ns; clk <= '1'; wait for 5 ns;
    valid_in <= '0';
    for i in 6 downto 0 loop
        clk <= '0'; wait for 5 ns;
        clk <= '1'; wait for 5 ns;
    end loop;
end loop;


end process;
end tb_arch;
```

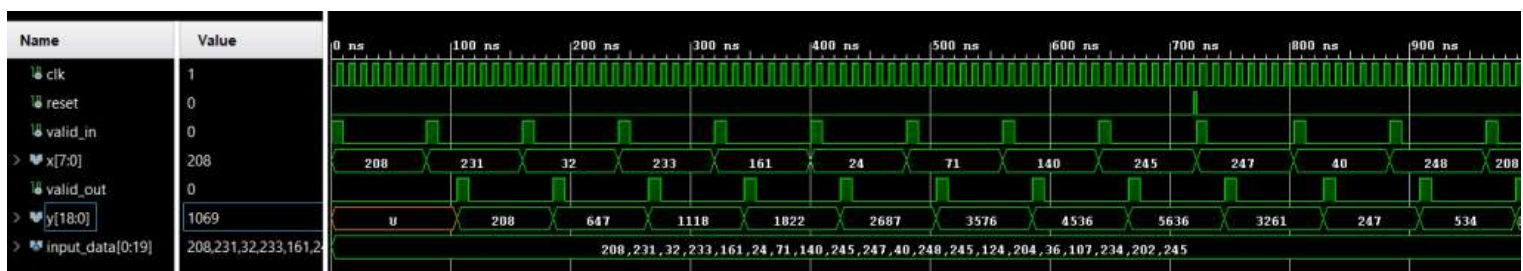→ Το αποτέλεσμα της προσομοίωσης φαίνεται στο παρακάτω σχήμα:



→ Οι πόροι που χρησιμοποιήθηκαν και η ισχύς που καταναλώνεται:

Resource	Utilization	Available	Utilization %
LUT	99	17600	0.56
FF	124	35200	0.35
IO	31	100	31.00

 

## 4η εργαστηριακή άσκηση

Power estimation from Synthesized netlist. Activity derived from constraints files, simulation files or vectorless analysis. Note: these early estimates can change after implementation.

**Total On-Chip Power:** **13.259 W (Junction temp exceeded!)**

**Design Power Budget:** **Not Specified**

**Power Budget Margin:** **N/A**

**Junction Temperature:** **125,0°C**

Thermal Margin: **-92,9°C (-7,5 W)**


Effective  $\theta_{JA}$ : **11,5°C/W**

Power supplied to off-chip devices: **0 W**

Confidence level: **Low**

[Launch Power Constraint Advisor](#) to find and fix invalid switching activity

### On-Chip Power

 

- Το κρίσιμο μονοπάτι είναι από την έξοδο της ROM μέχρι τον καταχωρητή που αποθηκεύουμε το επιμέρους άθροισμα σε κάθε κύκλο
- Το κρίσιμο μονοπάτι παρουσιάζει καθυστέρηση 6.234 ns, επομένως η συχνότητα λειτουργίας του FPGA είναι  $\frac{1}{6.234 \times 10^{-9}} = 160.42 \text{ MHz}$

